
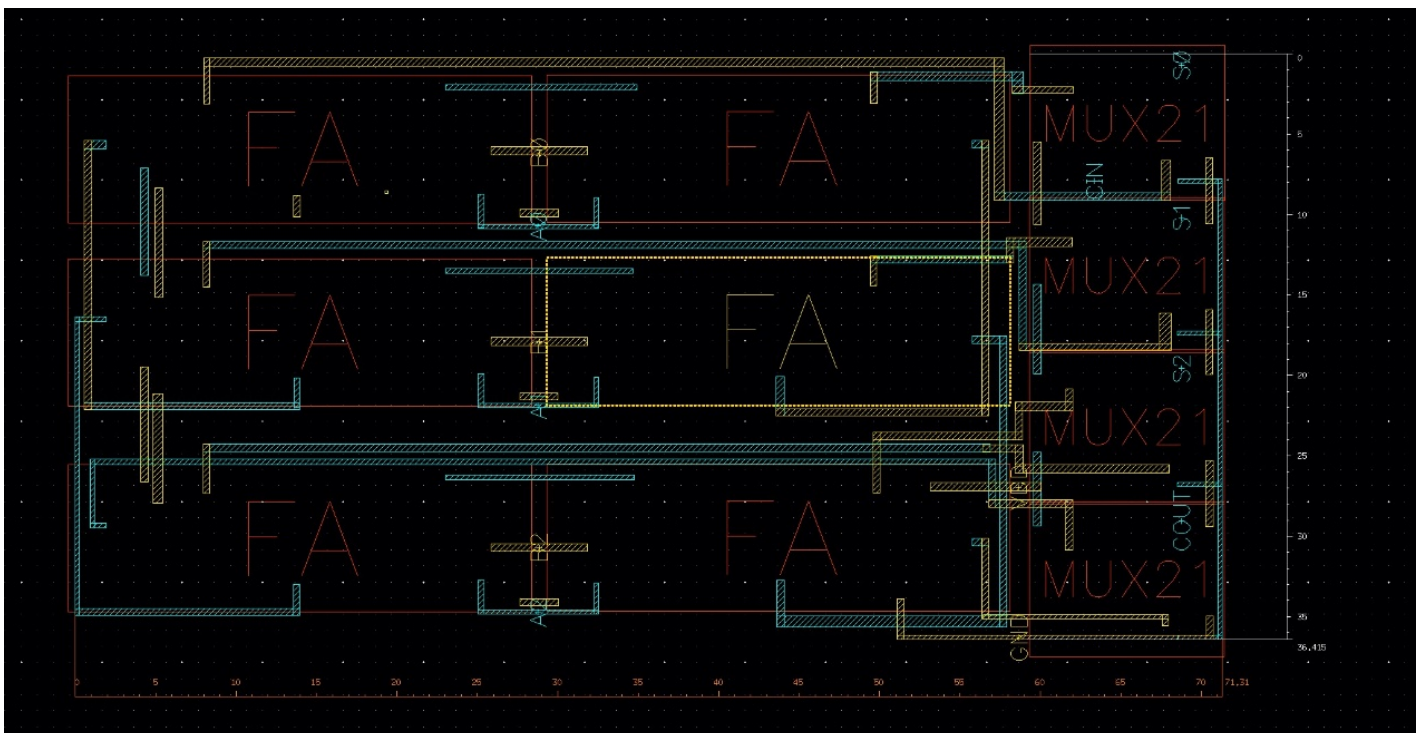


## Report 2



108062135 呂佳恩

### 1. Screenshots



Screenshot of ADDER3

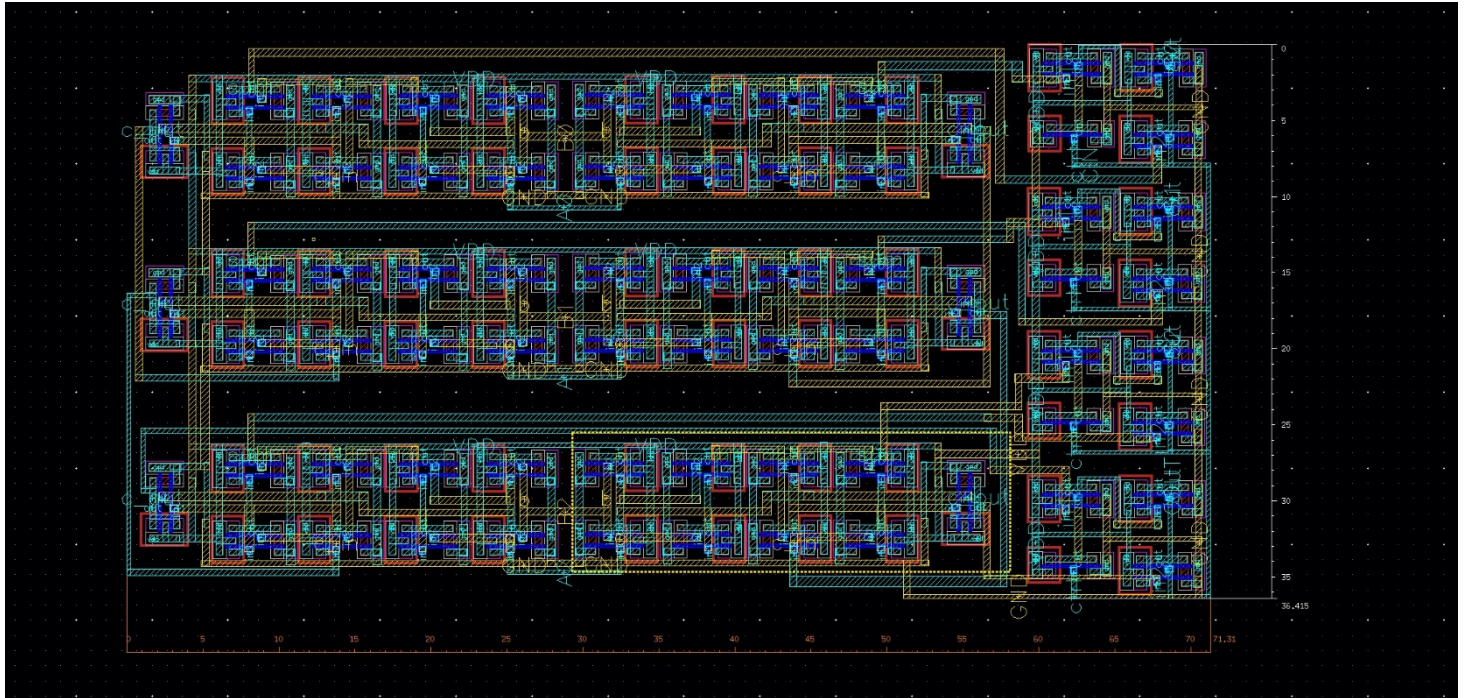

Screenshot of FA

 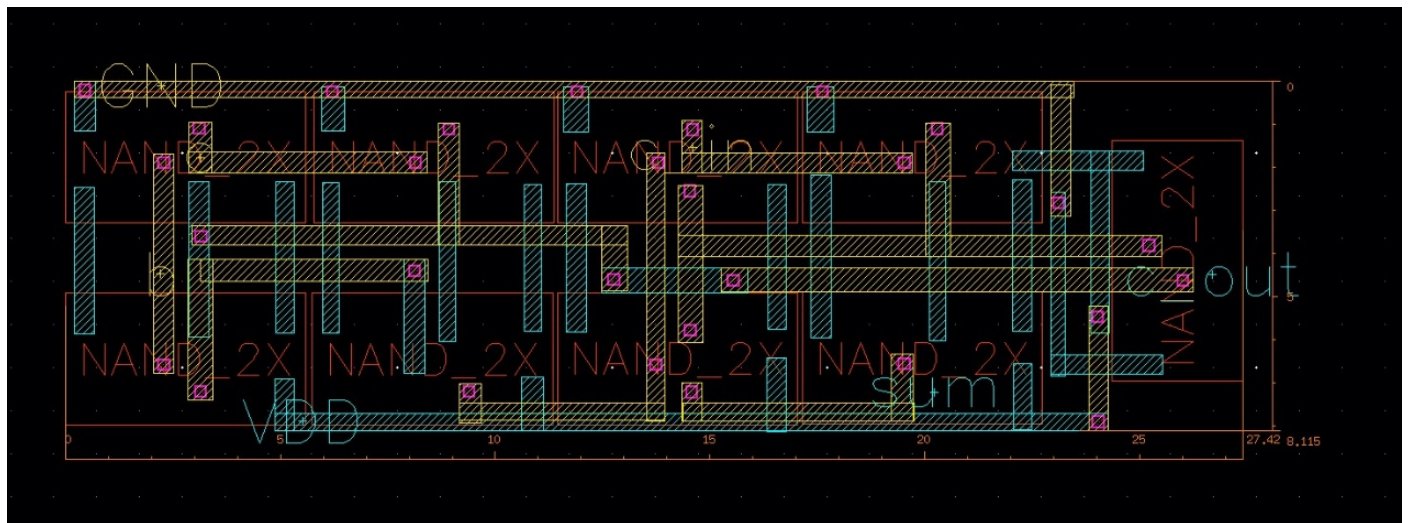


Screenshot of MUX

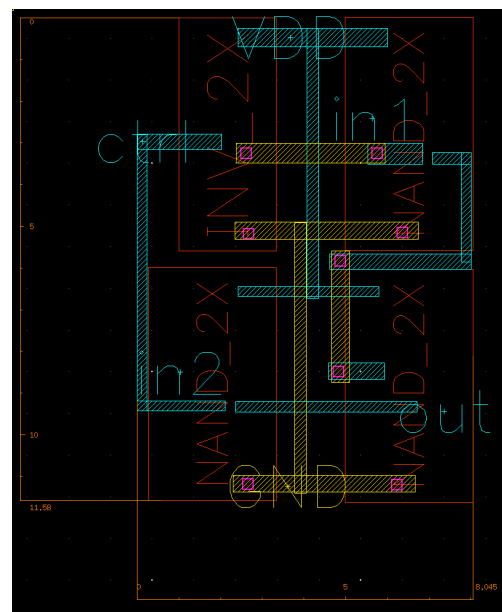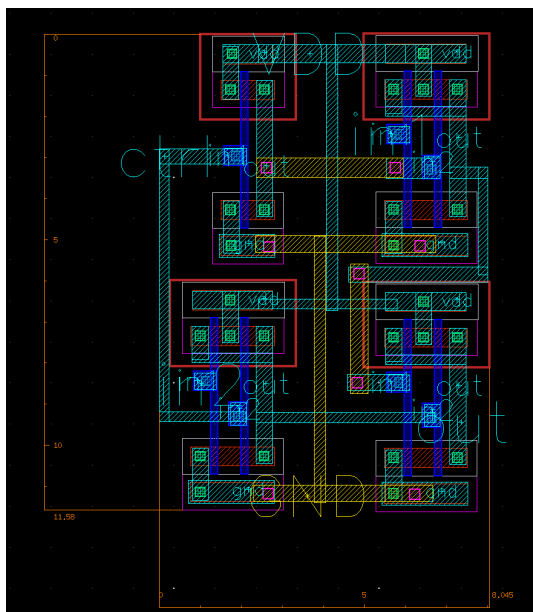




## Screenshot of DRC summary report

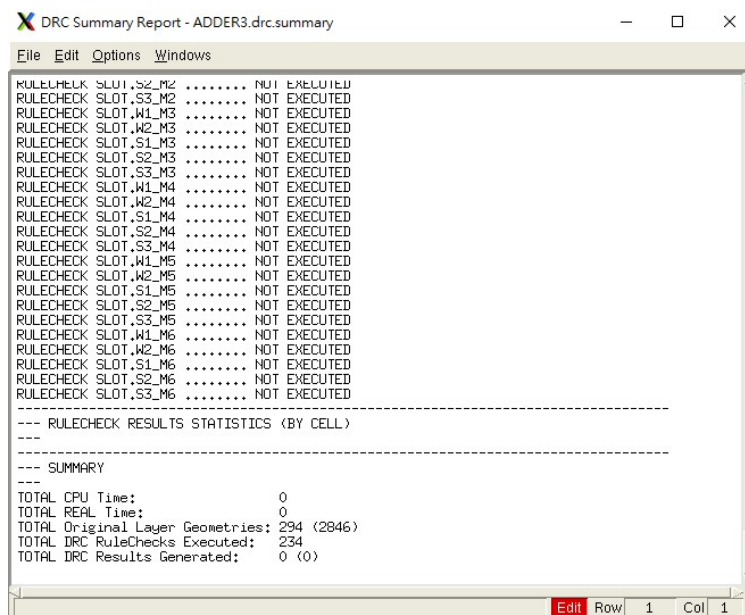

## Screenshot of LVS report

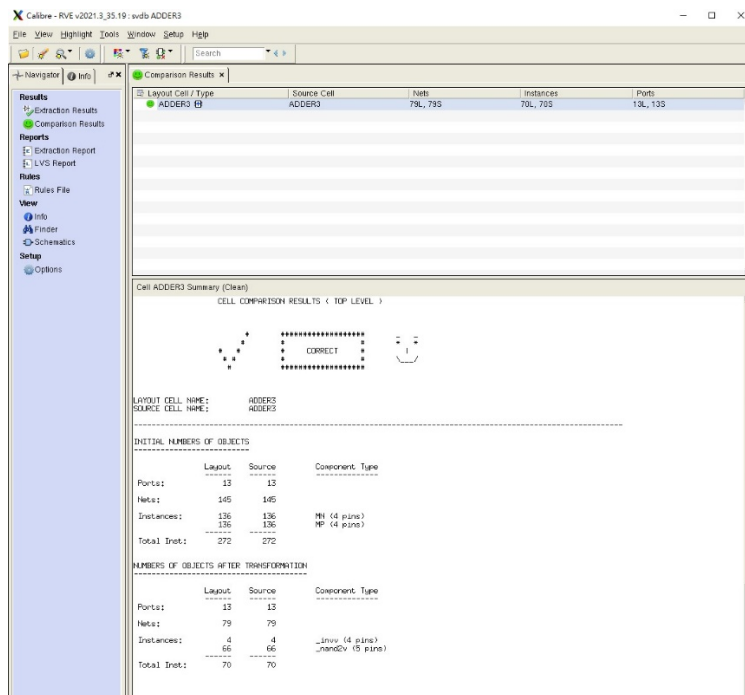

## Screenshot of LVS schematic of Adder3.src.net

```

ADDER3.src.net - 記事本
檔案(F) 編輯(E) 格式(O) 檢視(V) 說明
.subckt ADDER3 A0 A1 A2 B0 B1 B2 CIN S0 S1 S2 COUT VDD GND
x_FA1 A0 B0 GND SUM0 COUT0 VDD GND FA
x_FA2 A1 B1 COUT0 SUM1 COUT1 VDD GND FA
x_FA3 A2 B2 COUT1 SUM2 COUT2 VDD GND FA
x_FA4 A0 B0 VDD SUM00 COUT00 VDD GND FA
x_FA5 A1 B1 COUT00 SUM11 COUT11 VDD GND FA
x_FA6 A2 B2 COUT11 SUM22 COUT22 VDD GND FA
x_MUX1 COUT2 COUT22 CIN COUT VDD GND MUX21
x_MUX2 SUM00 SUM0 CIN S0 VDD GND MUX21
x_MUX3 SUM11 SUM1 CIN S1 VDD GND MUX21
x_MUX4 SUM22 SUM2 CIN S2 VDD GND MUX21
.ends

.subckt FA a b c_in sum c_out VDD GND
x_NAND1 a b tmp1 VDD GND NAND_2X
x_NAND2 a tmp1 tmp2 VDD GND NAND_2X
x_NAND3 b tmp1 tmp3 VDD GND NAND_2X
x_NAND4 tmp2 tmp3 tmp4 VDD GND NAND_2X
x_NAND5 tmp4 c_in tmp5 VDD GND NAND_2X
x_NAND6 tmp4 tmp5 tmp6 VDD GND NAND_2X
x_NAND7 tmp5 c_in tmp7 VDD GND NAND_2X
x_NAND8 tmp6 tmp7 sum VDD GND NAND_2X
x_NAND9 tmp5 tmp1 c_out VDD GND NAND_2X
.ends

.subckt MUX21 in1 in2 ctrl out VDD GND
x_in1_ctrlinv_nand in1 ctrl ctrl_inv_out sel1_out VDD GND NAND_2X
x_inv1 ctrl ctrl_inv_out sel1_out VDD GND INV_2X
x_in2_ctrl_nand in2 ctrl sel2_out VDD GND NAND_2X
x_sel12_nand sel1_out sel2_out out VDD GND NAND_2X
.ends

.subckt NAND_2X in1 in2 out vdd gnd
mp1 out in1 vdd vdd P_18 w=0.47u l=0.18u
mp2 out in2 vdd vdd P_18 w=0.47u l=0.18u
mn1 net in1 gnd gnd N_18 w=0.47u l=0.18u
mn2 out in2 net gnd N_18 w=0.47u l=0.18u
.ends

.subckt INV_2X in out vdd gnd
mp1 out in vdd vdd P_18 w=0.47u l=0.18u
mn1 out in gnd gnd N_18 w=0.47u l=0.18u
.ends

```

### 2. What else did I do to enhance my layout quality?

I started with the idea of making the design of FA and MUX easy to use in FA, so the output placement was crucial when I began the design. Also, the VDD and GND placement was place into consideration when the initial design was started. Also, I sometimes flipped the design as it would benefit the routing of the total design.

### 3. What have you learned from this homework?

I have a deep understanding of how Virtuoso works, and during the process of doing the homework, I have a better understanding of all things that need to be considered when doing designs, it made me appreciate the work of others more.

### 4. What problems have you encountered in this homework?

The main problem I encountered is that I don't know whether a placement would cause problems in the future or not. Also, small problems cascade into bigger ones as the layout scales. This made me have to go back to re-arrange the layouts that I first placed again and again, which was very time consuming.