

## Chapter 1

# Logic Design with MOSFET

何宗易

Tsung-Yi Ho

[tyho@cs.nthu.edu.tw](mailto:tyho@cs.nthu.edu.tw)

<http://theta.cs.nthu.edu.tw>

Department of Computer Science

National Tsing Hua University

Hsinchu, Taiwan




**Sabin Mathew, Founder  
Learn Engineering**



# nMOS Transistor


- Four terminals: gate, source, drain, body
- Gate – oxide – body stack looks like a capacitor
  - Gate and body are conductors
  - $\text{SiO}_2$  (oxide) is a very good insulator
  - Called metal – oxide – semiconductor (MOS) capacitor
  - Even though gate is no longer made of metal\*

\* Metal gates are returning today!

 

 
# nMOS Operation

- Body is usually tied to ground (0 V)
- When the gate is at a low voltage:
  - P-type body is at low voltage
  - Source-body and drain-body diodes are OFF
  - No current flows, transistor is OFF



 
# nMOS Operation Cont.

- When the gate is at a high voltage:
  - Positive charge on gate of MOS capacitor
  - Negative charge attracted to body
  - Inverts a channel under gate to n-type
  - Now current can flow through n-type silicon from source through channel to drain, transistor is ON


 
# pMOS Transistor


- Similar, but doping and voltages reversed
  - Body tied to high voltage ( $V_{DD}$ )
  - Gate low: transistor ON
  - Gate high: transistor OFF
  - Bubble indicates inverted behavior



 
# Signals and Wires

---


- Signals
  - $0 = V_{ss} = \text{Ground} = \text{GND} = \text{Low} = 0V$
  - $1 = V_{dd} = \text{Power} = \text{PWR} = \text{High} = 5V, 3.3V, 1.5V, 1.2V, 1.0V, \text{ etc.}$



- Wires

 

No connection


 


Connection



# Ideal Switches

---



- Switch

  

- Assert-high switch (nMOS)

  

- Assert-low switch (cMOS)

  



 
# Transistors as Switches


---

- We can view MOS transistors as electrically controlled switches
- Voltage at gate controls path from source to drain



# Series/Parallel Connections of Switches

- Series

 


AND operation

(y is defined only when  $a = 1$  and  $b = 1$ )

(y is undefined if  $a = 0$  or  $b = 0$ )

a	b	y
0	0	undefined
0	1	
1	0	
1	1	x

- Parallel

 

OR operation

(y is defined only when  $a = 1$  or  $b = 1$ )

(y is undefined if  $a = 0$  and  $b = 0$ )


a	b	y
0	0	undefined
0	1	x
1	0	
1	1	

# Inverter Design with Switches

---



- Inverter
  - The output is defined both when  $a = 0$  and when  $a = 1$ .

$a$	$y$
0	1
1	0

 



# CMOS Inverter

A	Y
0	1
1	0

  

# CMOS NAND Gate



A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

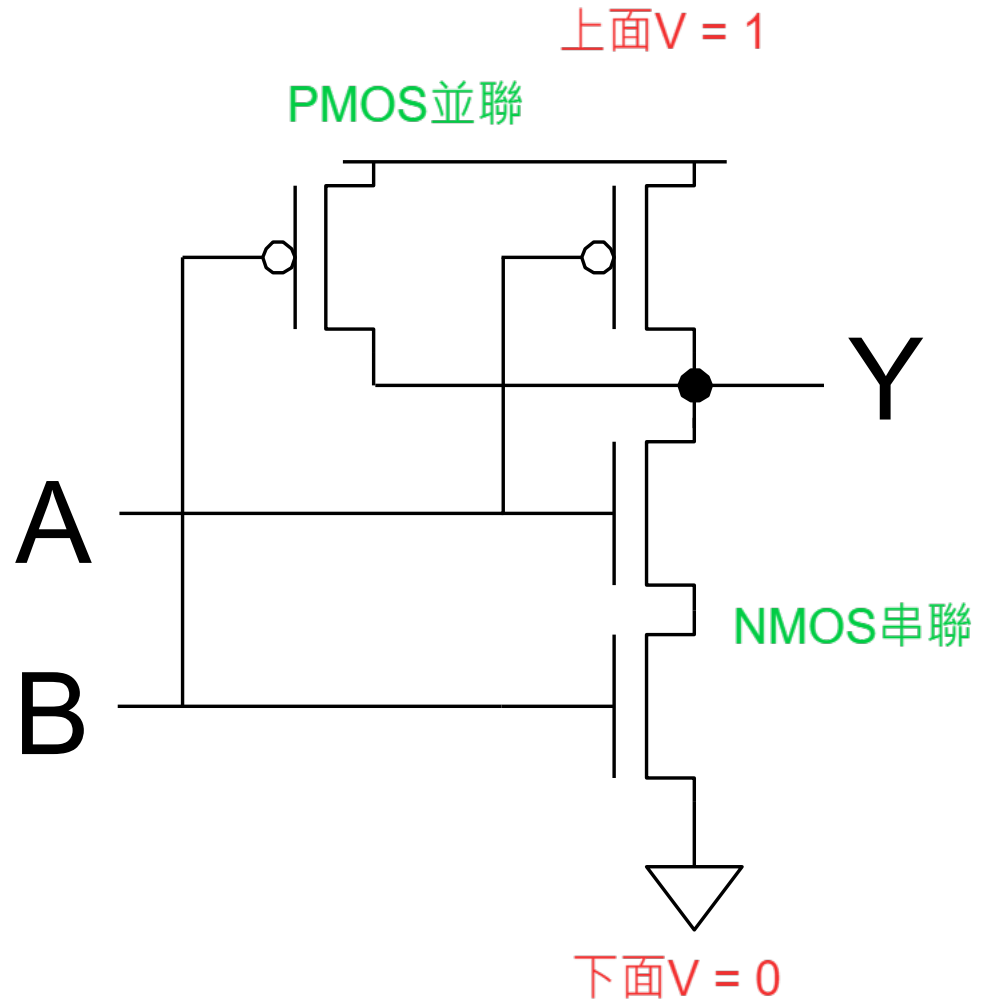 

# CMOS NOR Gate

(上面接V<sub>DD</sub>一定是PMOS, 下面GND一定是NMOS)


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

  
 
# 3-input NAND Gate

---


- Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0



# Complementary CMOS

- Complementary CMOS logic gates
  - nMOS *pull-down network*
  - pMOS *pull-up network*
  - a.k.a. static CMOS

pull-down: GND  
pull-up: V<sub>DD</sub>

 


	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (crowbar)


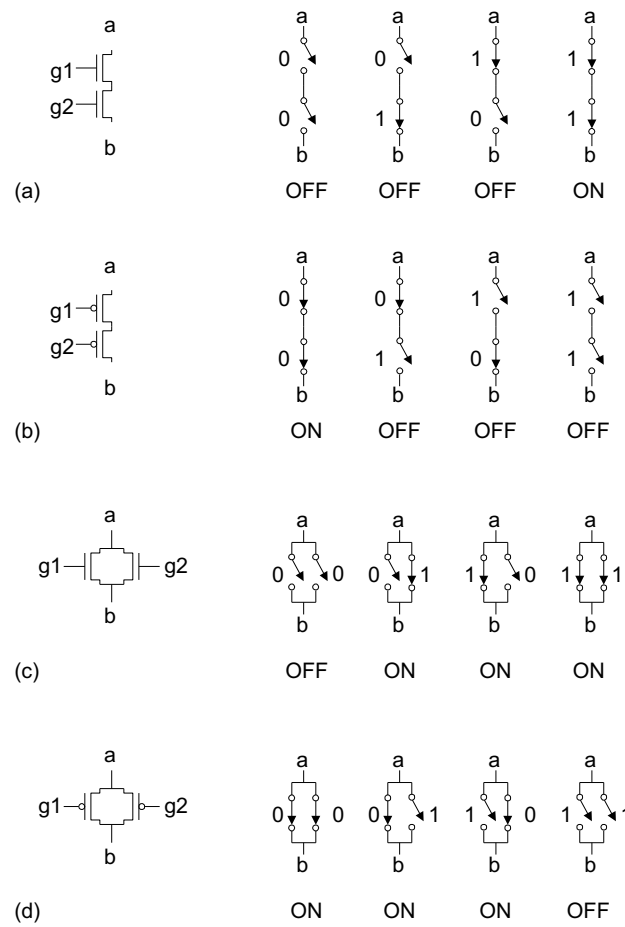
# Series and Parallel


- nMOS: 1 = ON
- pMOS: 0 = ON
- *Series*: both must be ON
- *Parallel*: either can be ON


 
# Conduction Complement

---

- Complementary CMOS gates always produce 0 or 1
- Ex: NAND gate
  - Series nMOS:  $Y=0$  when both inputs are 1
  - Thus  $Y=1$  when either input is 0
  - Requires parallel pMOS
- Rule of *Conduction Complements*
  - Pull-up network is complement of pull-down
  - Parallel  $\rightarrow$  series, series  $\rightarrow$  parallel






# Compound Gates

- *Compound gates* can do any inverting function
- Ex:

$$Y = \overline{A \cdot B + C \cdot D} \text{ (AND-AND-OR-INVERT, AOI22)}$$




   (1) ignore complement,  
然後做complement底下的  
expression=>NMOS  
(2) PMOS則做相反  
=> and改or, or改and



# Example: O3AI


$$Y = \overline{(A + B + C) \cdot D}$$

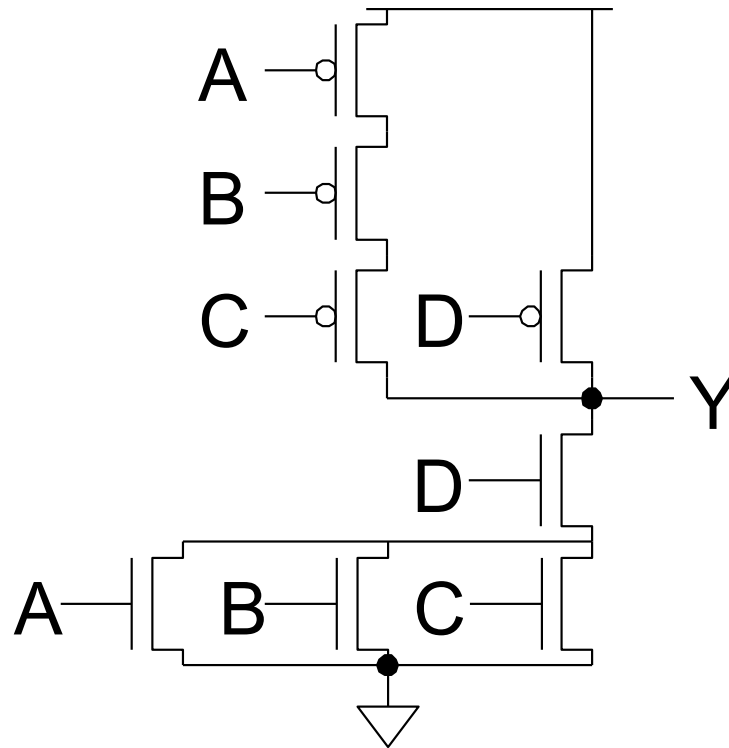

(1) ignore complement · 做  
 $(A+B+C) \cdot D \Rightarrow$  NMOS  
(2) 接著做PMOS  $\Rightarrow$   
or改and, and改or  $\Rightarrow$   
 $(A \cdot B \cdot C) + D$

# nFET Threshold voltages

- MOSFET has a characterizing parameter called the **threshold voltage**  $V_T$ .
- $V_T$  is established during **manufacturing process** and is assumed to be a given value to the **designer**.
- nFET has a threshold voltage  $V_{Tn}$  a positive number (0.5V~0.7V).

 

**Figure 2.14** Threshold voltage of an nFET


# nFET Threshold voltages

---

- If  $V_{GSn} \leq V_{Tn}$  the transistor acts like an open circuit. A transistor is OFF.
  - The drain terminal is the one close to Vdd and the source terminal is the one connected to Gnd.
- If  $V_{GSn} \geq V_{Tn}$  the nFET drain and source are connected. A transistor is ON.

# pFET Threshold voltages


- A pFET behaves in a complementary manner.  $V_{Tp}$  is a negative number (-0.5V~-0.8V). We use  $V_{SGp} = -V_{GSp}$
- If  $V_{SGp} \leq |V_{Tp}|$ , the transistor acts like an open circuit. A transistor is OFF.
- If  $V_{SGp} \geq |V_{Tp}|$ , the pFET drain and source are connected. A transistor is ON.

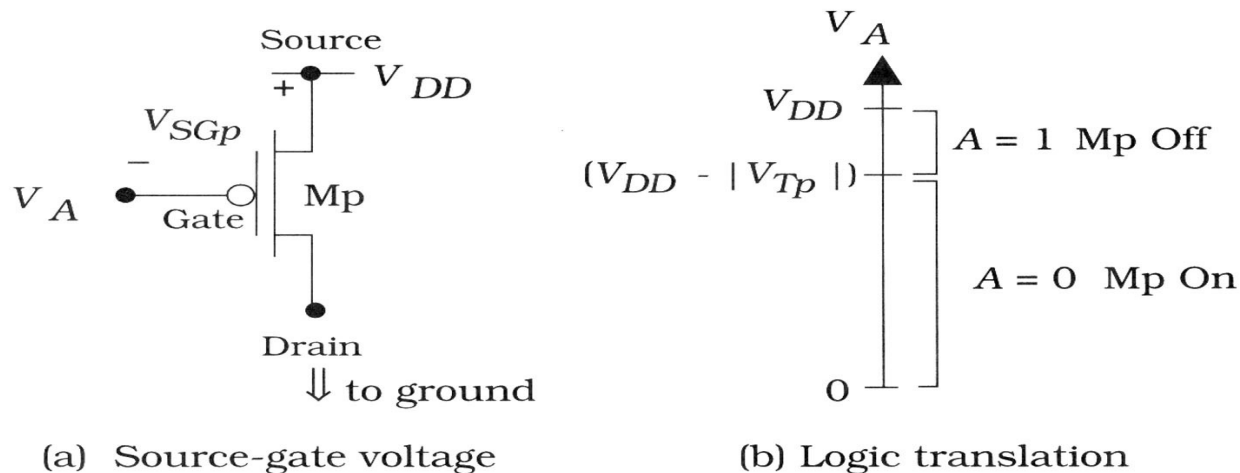


**Figure 2.15** pFET threshold voltage
 
# Pass Characteristics (nFET)

- Ideal electrical switch can pass any voltage.
- The pass characteristics of nFET.
  - Fig 2.16a, a logic 0 is connected from left to the right.
  - Fig 2.16b, a  $V_{DD}$  is applied in the left. The output voltage is reduced to a value  $V_{DD} - V_{Tn}$ . (Threshold voltage loss)
  - nFET can only pass a weak logic 1 but strong logic 0.



(a) Logic 0 transfer

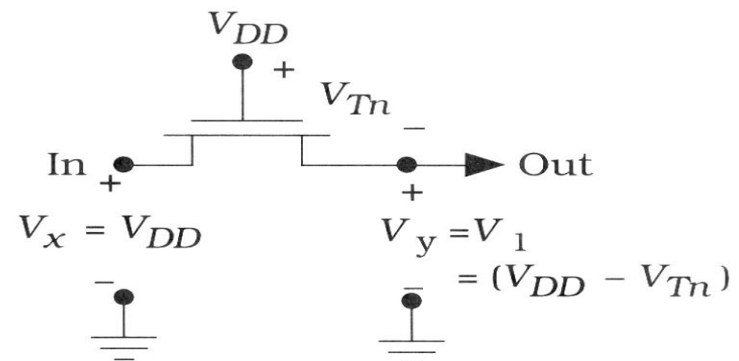


(b) Logic 1 transfer

**Figure 2.16** nFET pass characteristics




# Pass Characteristics (pFET)

- The pass characteristics of pFET.
  - Fig 2.17a, a logic 1 is connected from left to the right.
  - Fig 2.17b, a VSS is applied in the right. The output voltage drops to a value  $|V_{Tp}|$  (Threshold voltage loss)
  - pFET can only pass a weak logic 0 but strong logic 1.

 

(a) Logic 1 transfer

 

(b) Logic 0 transfer

**Figure 2.17** pFET pass characteristics

# Signal Strength










---

- *Strength* of signal
  - How close it approximates ideal voltage source
- $V_{DD}$  and GND rails are strongest 1 and 0
- nMOS pass strong 0
  - But degraded or weak 1
- pMOS pass strong 1
  - But degraded or weak 0
- Thus nMOS are best for pull-down network

# Pass Transistors

---


- Transistors can be used as switches

         


# Transmission Gates

- Pass transistors produce degraded outputs
- *Transmission gates* pass both 0 and 1 well

NMOS, PMOS串在一起, g跟gb為dual訊號

 

$g = 0, gb = 1$

 

$g = 1, gb = 0$



Input




Output

$g = 1, gb = 0$

0  $\rightarrow$  strong 0

$g = 1, gb = 0$

1  $\rightarrow$  strong 1

  
 


# Tristates

- *Tristate buffer* produces Z when not enabled

=>with enable


EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

  
 
# Nonrestoring Tristate


---

- Transmission gate acts as tristate buffer
  - Only two transistors
  - But *nonrestoring*
    - Noise on A is passed on to Y


 
# Tristate Inverter

- Tristate inverter produces restored output
  - Violates conduction complement rule
  - Because we want a Z output




# Multiplexers

---

- 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1


 



  
# Gate-Level Mux Design

---


- $Y = SD_1 + \bar{S}D_0$  (too many transistors)
- How many transistors are needed?


 
# Transmission Gate Mux


---

- Nonrestoring mux uses two transmission gates
  - Only 4 transistors




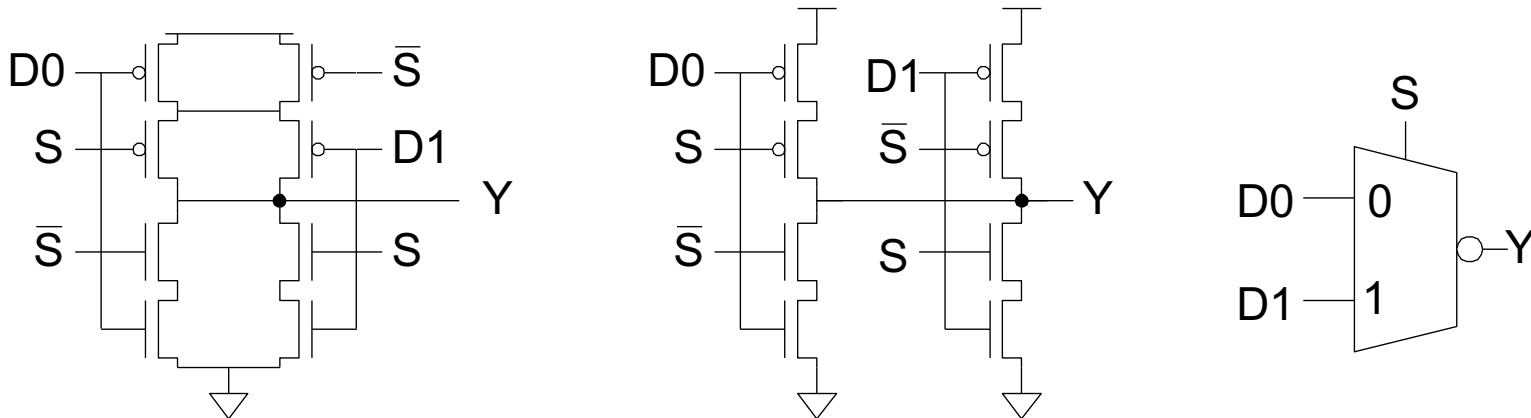
# Inverting Mux

- Inverting multiplexer
  - Use compound AOI22
  - Or pair of tristate inverters
  - Essentially the same thing
- Noninverting multiplexer adds an inverter



# 4:1 Multiplexer

 
 
- 4:1 mux chooses one of 4 inputs using two selects
  - Two levels of 2:1 muxes
  - Or four tristates


  
# D Latch

---



- When  $CLK = 1$ , latch is *transparent*
  - D flows through to Q like a buffer
- When  $CLK = 0$ , the latch is *opaque*
  - Q holds its old value independent of D
- a.k.a. *transparent latch* or *level-sensitive latch*



# D Latch Design

- Multiplexer chooses D or old Q



=> Set CLK as enable

  
  
# D Flip-flop


---

- When CLK rises, D is copied to Q
- At all other times, Q holds its value
- a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*



# D Flip-flop Design

- Built from master and slave D latches

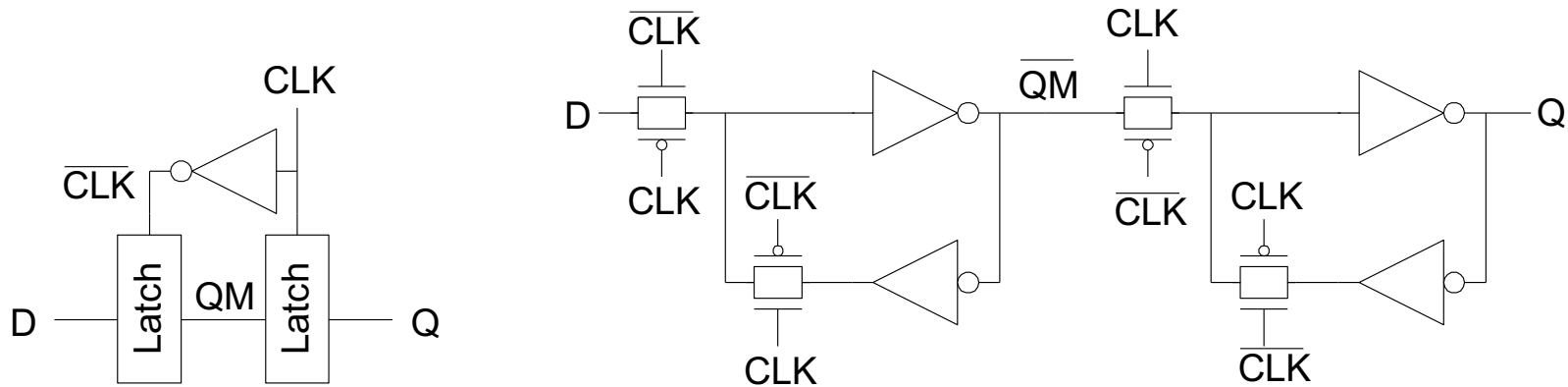




# CMOS Fabrication

---

- CMOS transistors are fabricated on silicon wafer
- Lithography process similar to printing press
- On each step, different materials are deposited or etched
- Easiest to understand by viewing both top and cross-section of wafer in a simplified manufacturing process

 
# Inverter Cross-section

- Typically use p-type substrate for nMOS transistors
- Requires n-well for body of pMOS transistors



 
# Well and Substrate Taps

- Substrate must be tied to GND and n-well to  $V_{DD}$
- Metal to lightly-doped semiconductor forms poor connection called Shottky Diode
- Use heavily doped well and substrate contacts / taps



 
# Inverter Mask Set

- Transistors and wires are defined by *masks*
- Cross-section taken along dashed line


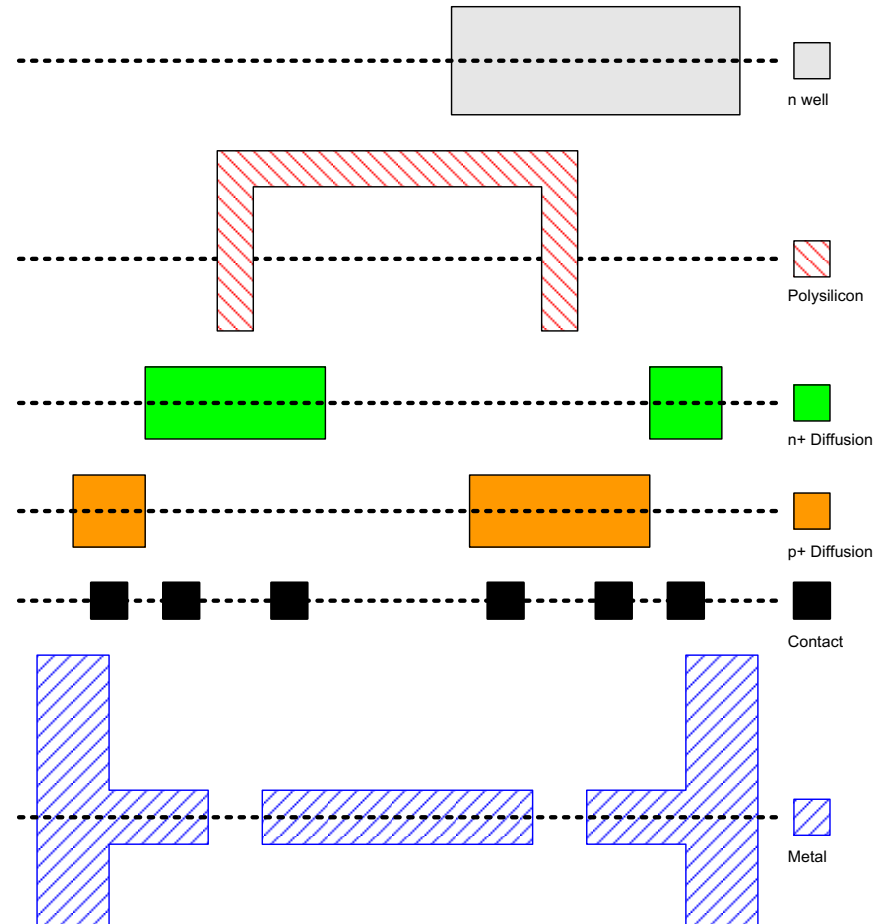
# Detailed Mask Views

- Six masks
  - n-well
  - Polysilicon
  - n+ diffusion
  - p+ diffusion
  - Contact
  - Metal  
(for 連線)



# Fabrication

---

- Chips are built in huge factories called fabs
- Contain clean rooms as large as football fields



Courtesy of International  
Business Machines Corporation.  
Unauthorized use not permitted.

# Fabrication Steps

---

- Start with blank wafer
- Build inverter from the bottom up
- First step will be to form the n-well
  - Cover wafer with protective layer of  $\text{SiO}_2$  (oxide)
  - Remove layer where n-well should be built
  - Implant or diffuse n dopants into exposed wafer
  - Strip off  $\text{SiO}_2$



p substrate

# Oxidation

---

- Grow  $\text{SiO}_2$  on top of Si wafer
  - 900 – 1200 C with  $\text{H}_2\text{O}$  or  $\text{O}_2$  in oxidation furnace





 
# Photoresist

---


- Spin on photoresist
  - Photoresist is a light-sensitive organic polymer
  - Softens where exposed to light


 
# Lithography

---


- Expose photoresist through n-well mask
- Strip off exposed photoresist


 
# Etch (蝕刻)

---


- Etch oxide with hydrofluoric acid (HF)
  - Seeps through skin and eats bone; nasty stuff!!!
- Only attacks oxide where resist has been exposed


 
# Strip Photoresist

---


- Strip off remaining photoresist
  - Use mixture of acids called piranah etch
- Necessary so resist doesn't melt in next step


 
# n-well

---

- n-well is formed with **diffusion or ion implantation**
- Diffusion
  - Place wafer in furnace with arsenic gas
  - Heat until As atoms diffuse into exposed Si
- Ion Implantation
  - Blast wafer with beam of As ions
  - Ions blocked by  $\text{SiO}_2$ , only enter exposed Si



# Strip Oxide

---


- Strip off the remaining oxide using HF
- Back to bare wafer with n-well
- Subsequent steps involve similar series of steps


 
# Polysilicon

---


- Deposit very thin layer of gate oxide
  - $< 20 \text{ \AA}$  (6-7 atomic layers)
- Chemical Vapor Deposition (CVD) of silicon layer
  - Place wafer in furnace with Silane gas ( $\text{SiH}_4$ )
  - Forms many small crystals called polysilicon
  - Heavily doped to be good conductor


 
# Polysilicon Patterning

---

- Use same lithography process to pattern polysilicon





 
# Self-Aligned Process

---


- Use oxide and masking to expose where n+ dopants should be diffused or implanted
- N-diffusion forms nMOS source, drain, and n-well contact


 
# N-diffusion

---


- Pattern oxide and form n+ regions
- *Self-aligned process* where gate blocks diffusion
- Polysilicon is better than metal for self-aligned gates because it doesn't melt during later processing


 
# N-diffusion cont.

---


- Historically dopants were diffused
- Usually ion implantation today
- But regions are still called diffusion


 
# N-diffusion cont.


---

- Strip off oxide to complete patterning step


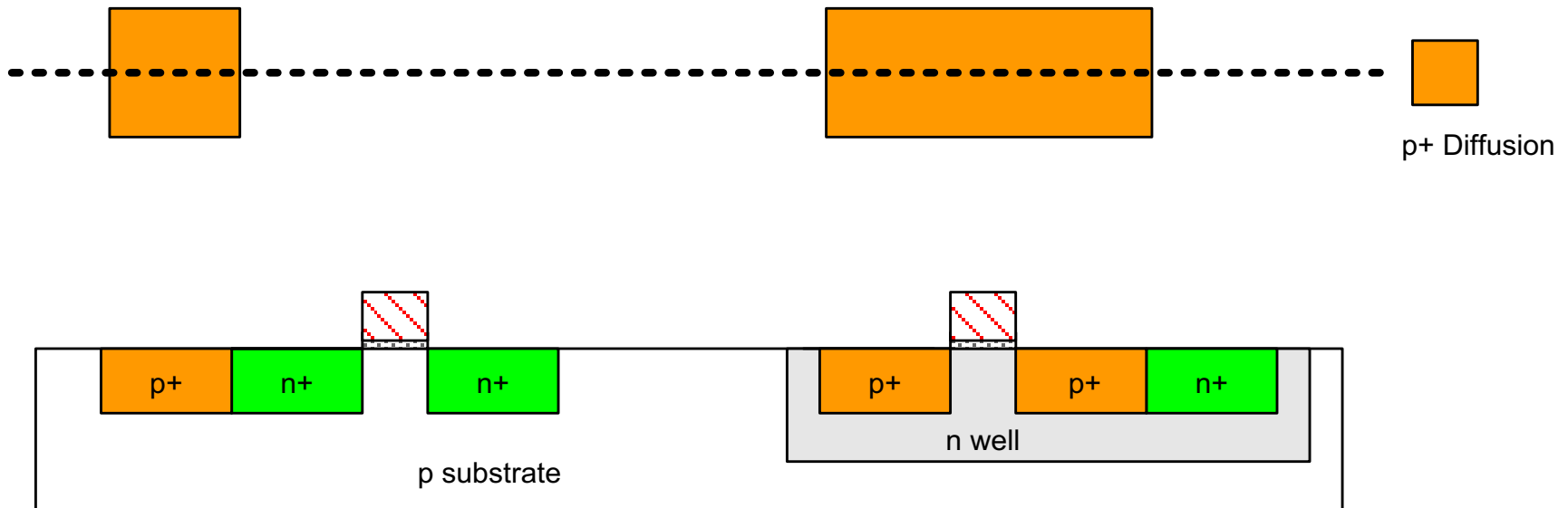
# P-Diffusion


- Similar set of steps form p+ diffusion regions for pMOS source and drain and substrate contact


 
# Contacts


---

- Now we need to wire together the devices
- Cover chip with thick field oxide
- Etch oxide where contact cuts are needed


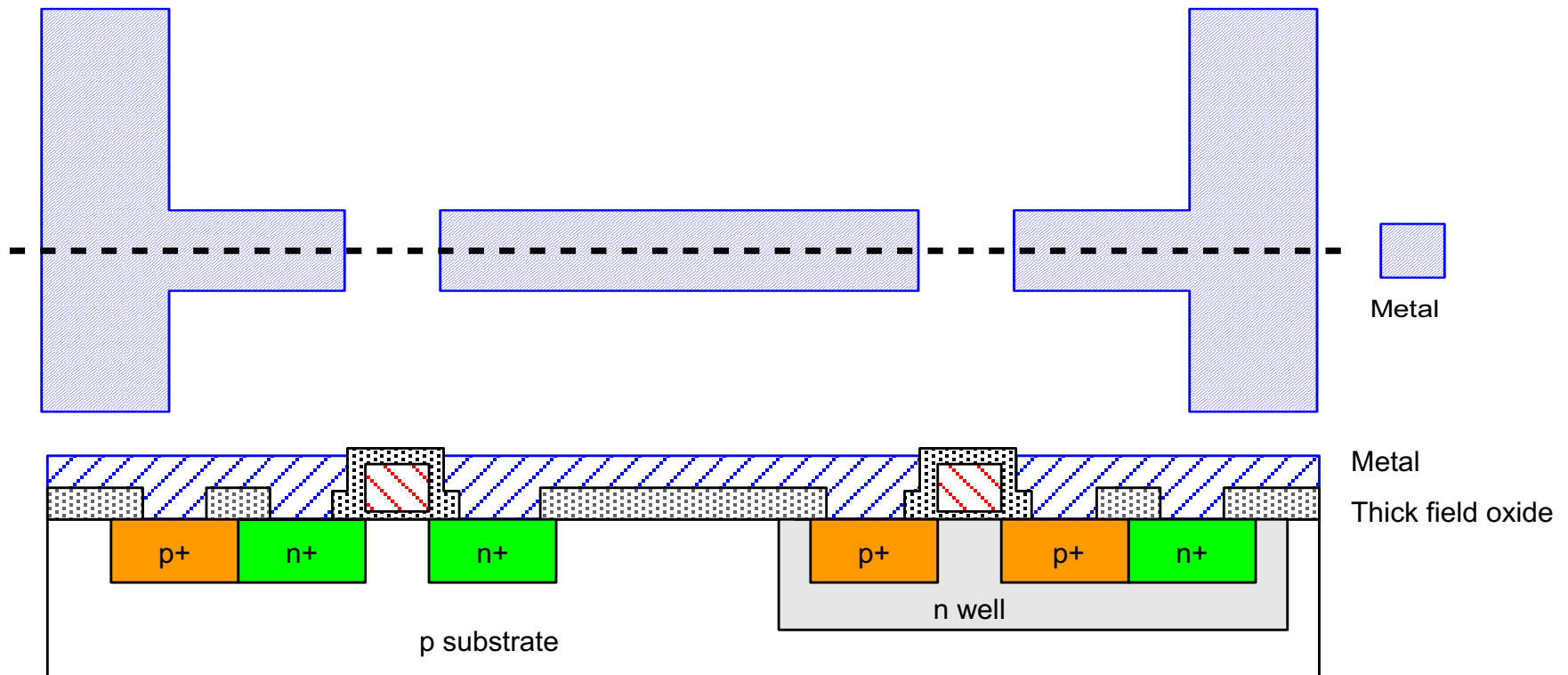
# Metalization

- Sputter on aluminum over whole wafer
- Pattern to remove excess metal, leaving wires



# Layout

---

- Chips are specified with set of masks
- Minimum dimensions of masks determine transistor size (and hence speed, cost, and power)
- Feature size  $f$  = distance between source and drain
  - Set by minimum width of polysilicon
- Feature size improves 30% every 3 years or so
- Normalize for feature size when describing design rules
- Express rules in terms of  $\lambda = f/2$ 
  - E.g.  $\lambda = 0.3 \mu\text{m}$  in  $0.6 \mu\text{m}$  process




# Gate Layout

---


- Layout can be very time consuming
  - Design gates to fit together nicely
  - Build a library of standard cells
- Standard cell design methodology
  - $V_{DD}$  and GND should abut (standard height) =>在相同高度
  - Adjacent gates should satisfy design rules
  - nMOS at bottom and pMOS at top
  - All gates include well and substrate contacts

(所有單一或複合式的gate都會存成library)

# Basic Gate Design

 


(a) Circuit

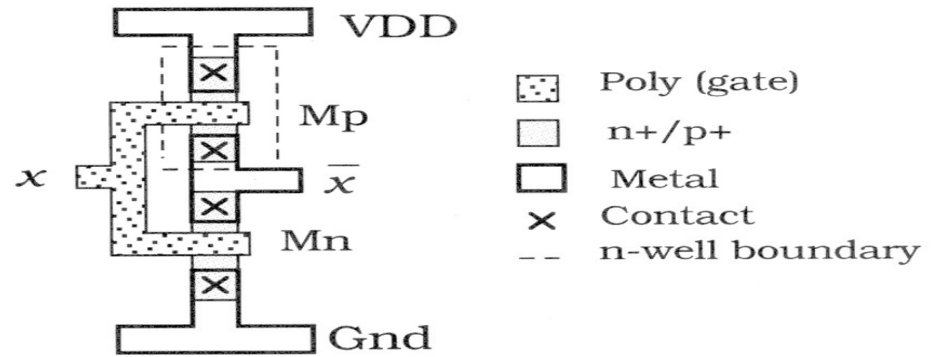


(b) Layer patterning

**Figure 3.31** Translating a NOT gate circuit to silicon

 

(a) Circuit

 


(b) Layer patterning

**Figure 3.32** Alternate layout for a NOT gate

 
# Stick Diagrams

- *Stick diagrams* help plan layout quickly
  - Need not be to scale
  - Draw with color pencils or dry-erase markers




# Example: Inverter

---

 


 
# Example: NAND3

- Horizontal N-diffusion and p-diffusion strips
- Vertical polysilicon gates
- Metal1  $V_{DD}$  rail at top
- Metal1 GND rail at bottom
- $32\lambda$  by  $40\lambda$



  
# Wiring Tracks

- A *wiring track* is the space required for a wire
  - $4\lambda$  width,  $4\lambda$  spacing from neighbor =  $8\lambda$  pitch
- Transistors also consume one wiring track



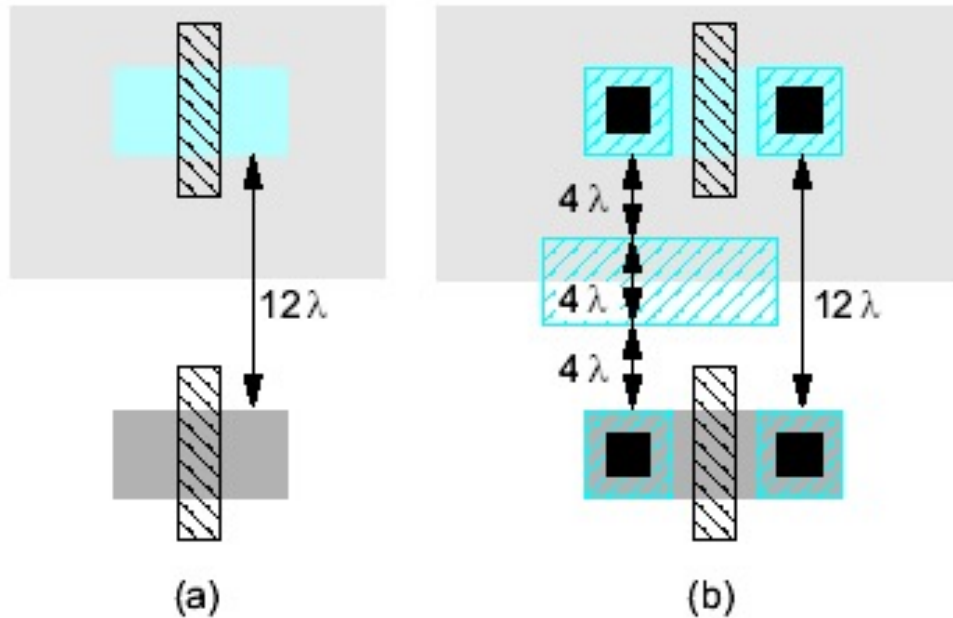
# Well spacing

- Wells must surround transistors by  $6\lambda$ 
  - Implies  $12\lambda$  between opposite transistor flavors
  - Leaves room for one wire track








 


(a) Logic diagram

 


(b) Layout

**Figure 3.34** Non-inverting buffer

 - Interconnect routing problems in layout.




(a) Logic diagram

 


(b) Layout

**Figure 3.35** Layout of a transmission gate with a driver

 


(a) Circuit

 


(b) Layer design

**Figure 3.36** NAND2 layout

 


(a) NOR3

 


(b) NAND3

**Figure 3.39** Layout for 3-input gates

 


(a) Circuit

 


### (b) Patterning

**Figure 3.40** Extension of layout technique to a complex logic gate

 


(a) Pattern

 


(b) Circuit

**Figure 3.41** Creation of the dual network

 

(a) Circuit

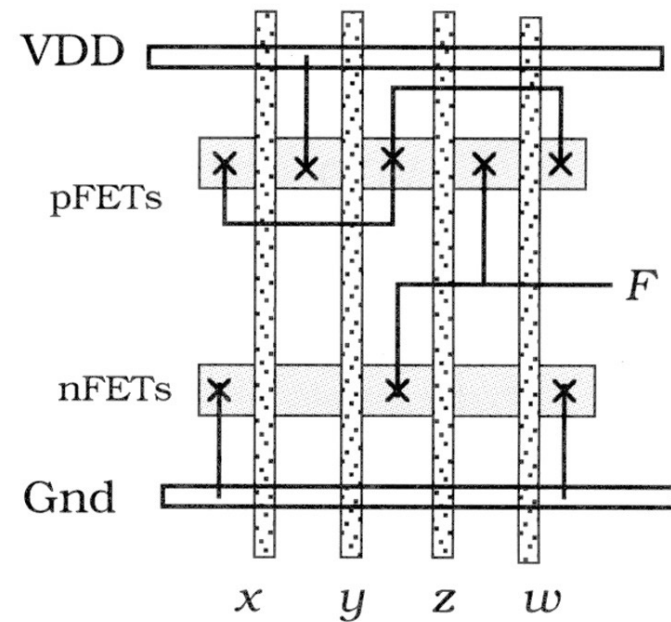


(b) Layout wiring

**Figure 3.42** A general 4-input AOI gate

# Example: O3AI

- Sketch a stick diagram for O3AI and estimate area


$$Y = \overline{(A + B + C)} \cdot D$$

 




$$F = \overline{(A+B+C).D}$$

What layout is faster and why?

 

Alternatively, do we connect point 1 or point 2 to GND?


Layout 1

 

Hint: How many drain capacitances do each of the layouts possess?

Does your choice differ if signal A is the first arriving signal?

Layout 2

 

# Summary

---

- MOS transistors are stacks of gate, oxide, silicon
- Act as electrically controlled switches
- Build logic gates out of switches
- Draw masks to specify layout of transistors
  
- Now you know everything necessary to start designing schematics and layout for a simple chip!

# Questions?